

ELECTRONIC VOTING MACHINE

Hardware Design Document

Submitted by Group 54

Isha Sethi


Jaskaran Singh Bhatia

Vivek Arora


Rohan Kumar

Vishal Amber Revanur

Date: 19th April, 2020

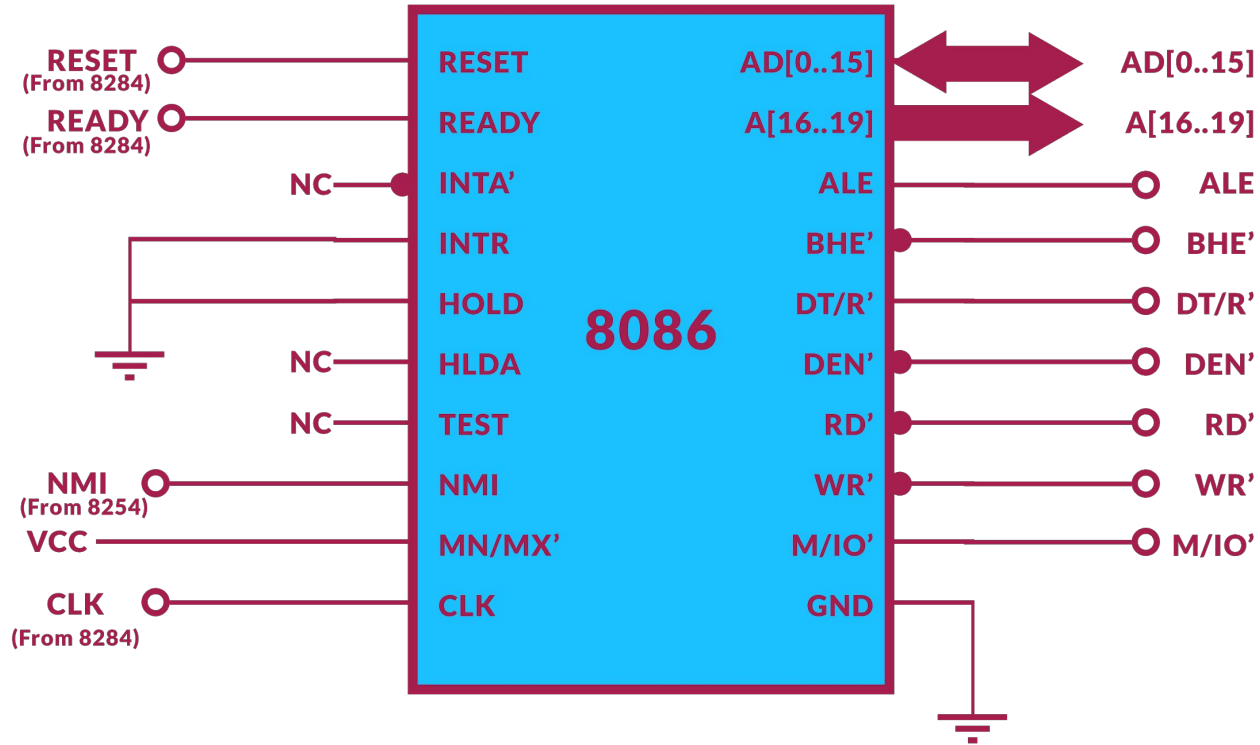

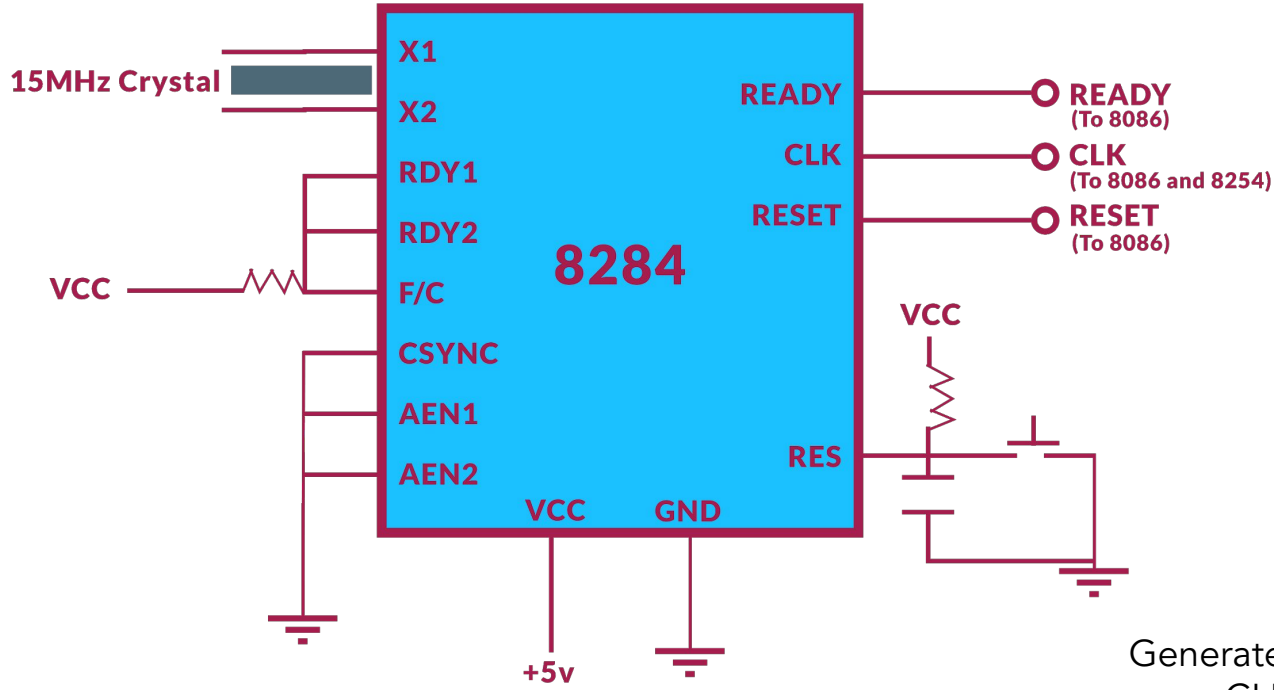
8086 Microprocessor with required connections



8284 Clock Generator


Generates:

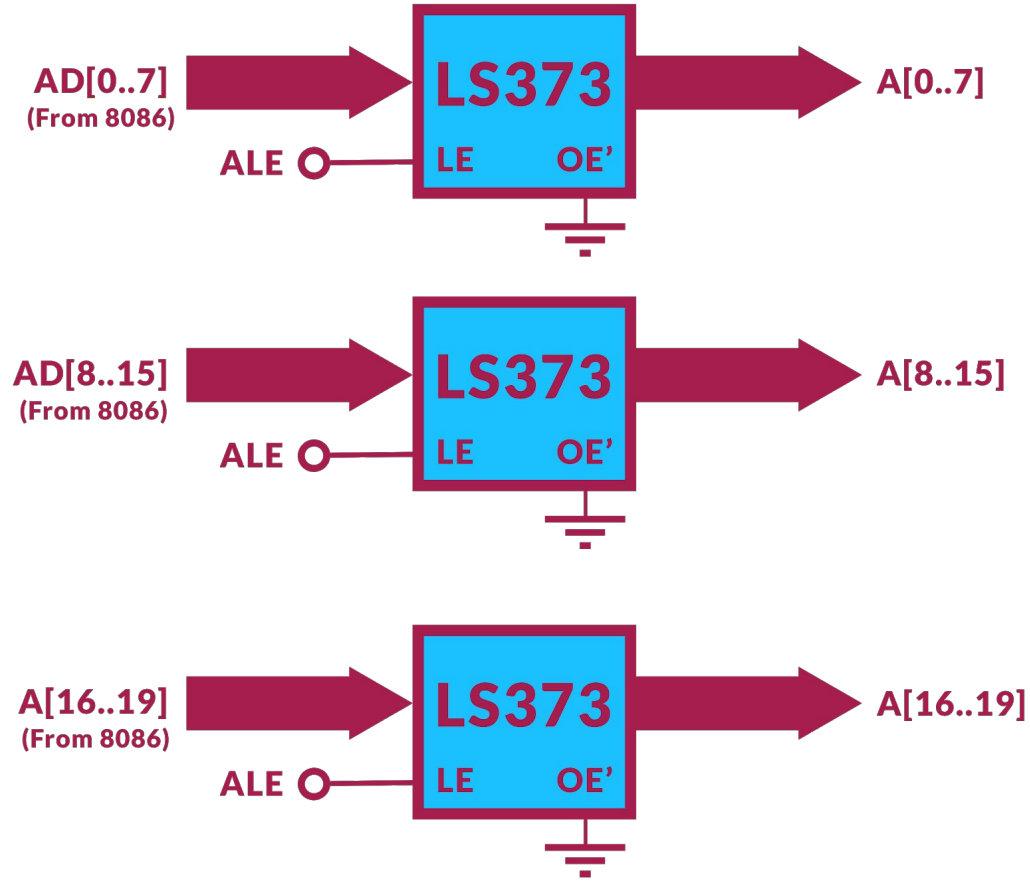- CLK @5Mhz
- PCLK @2.5Mhz
- RESET Signal on switch press




Address line Demultiplexing


Data line Demultiplexing

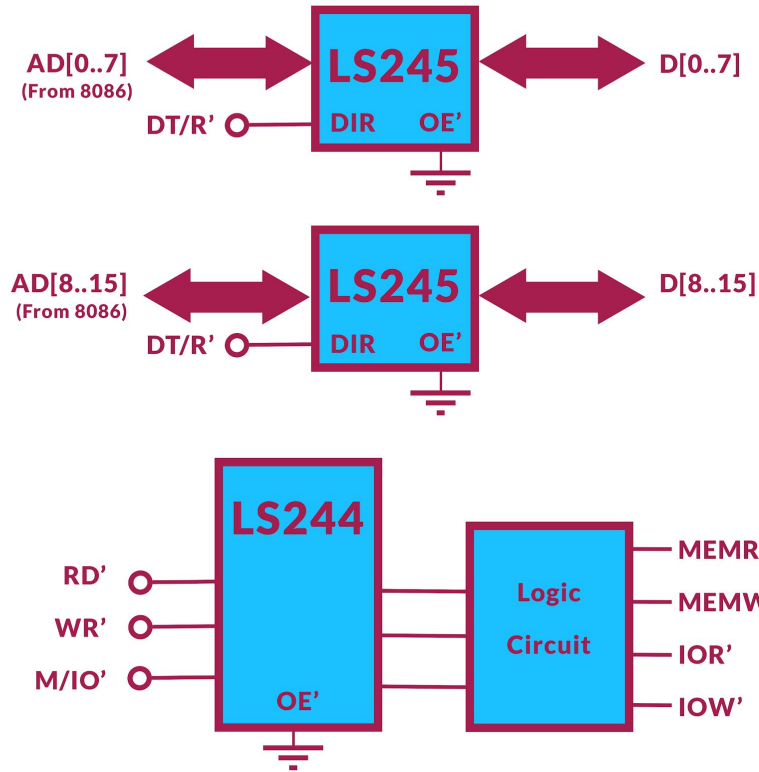





Control Line generation

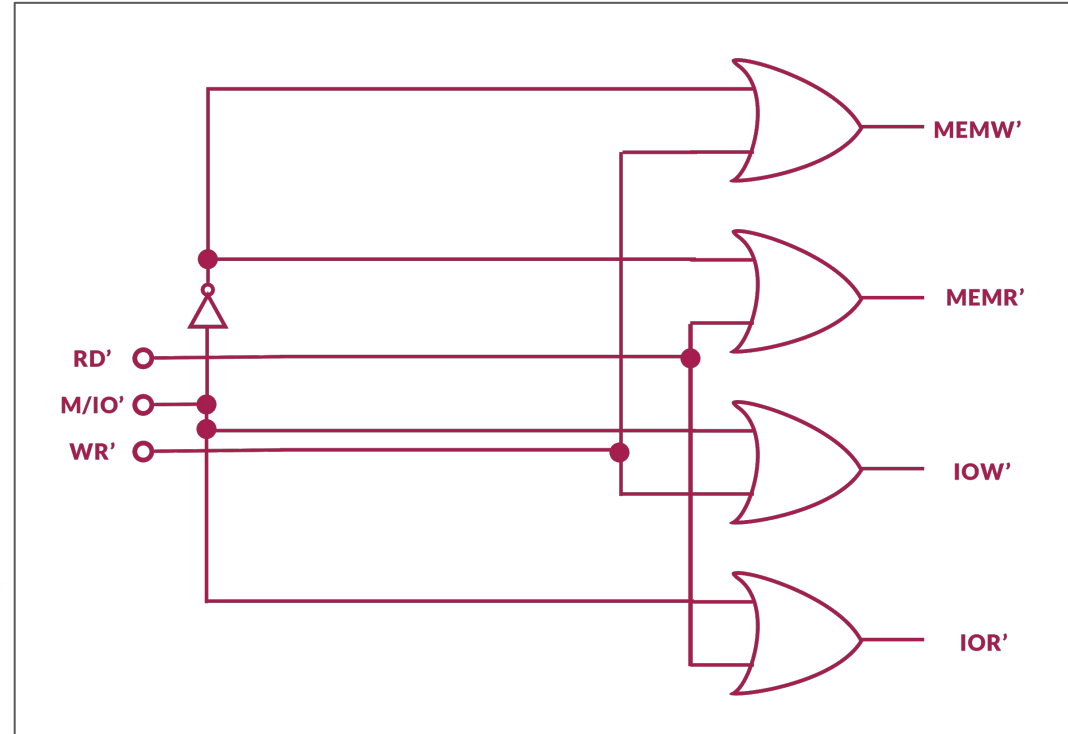

Logic Circuit as used

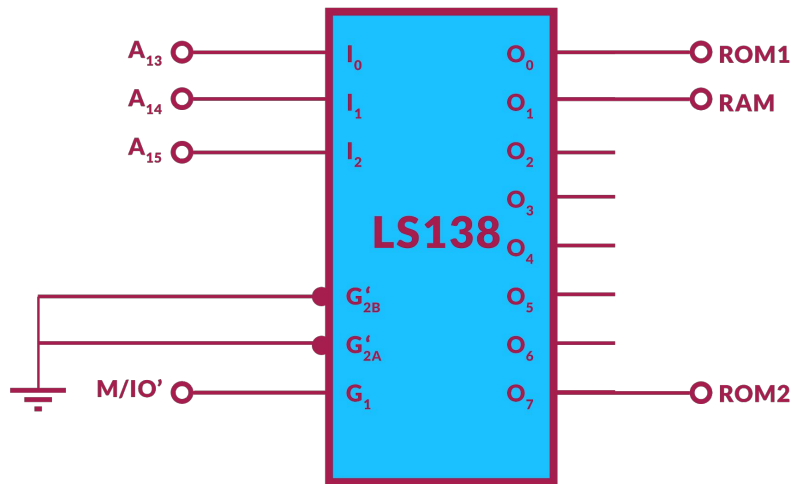

Control Line generation

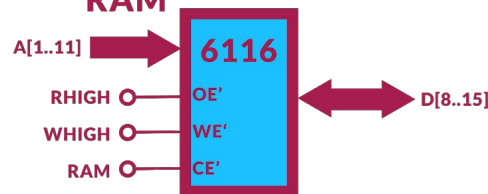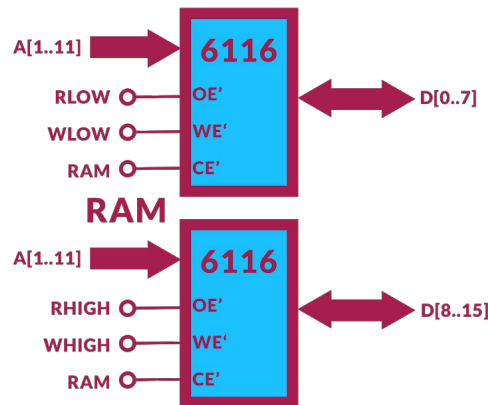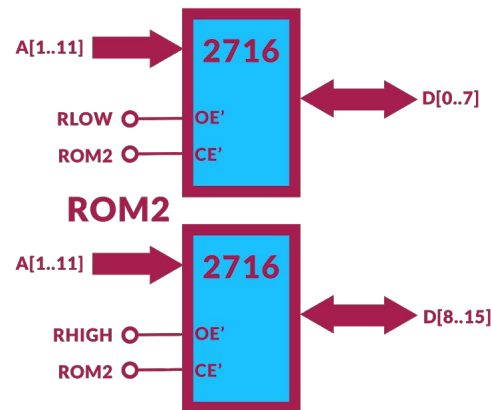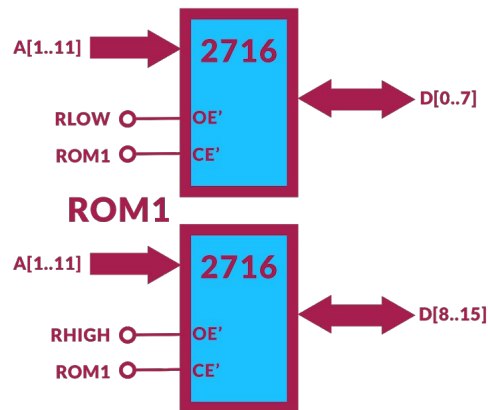


Memory Addresses:

ROM1: 00000h to 00FFFh

ROM2: 02000h to 02FFFh

RAM: FF000h to FFFFFh

Memory Chips

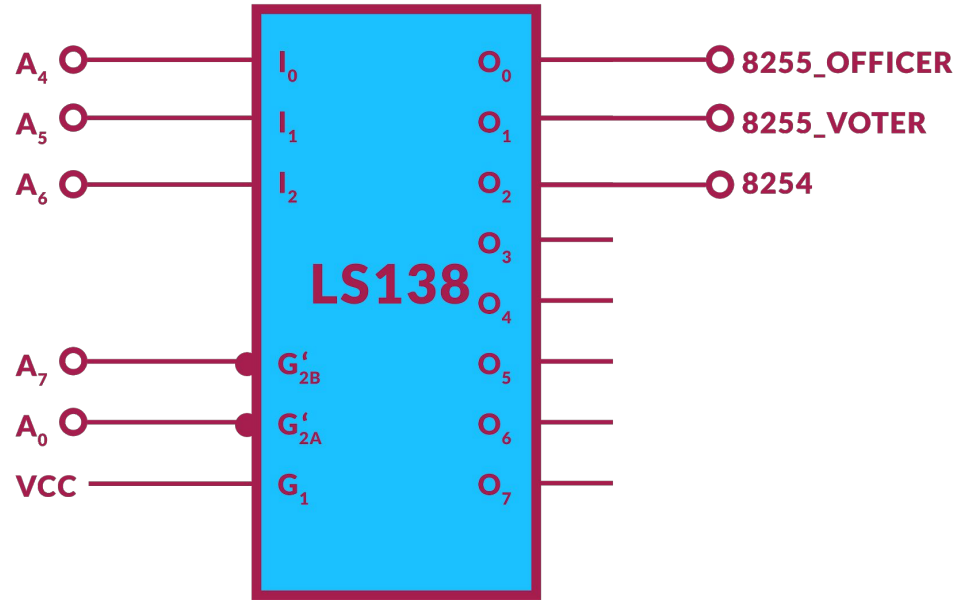


I/O Decoder

IO Addresses:

Officer Side 8255: 00h to 06h

Voter Side 8255: 10h to 16h

8254: 20h to 26h

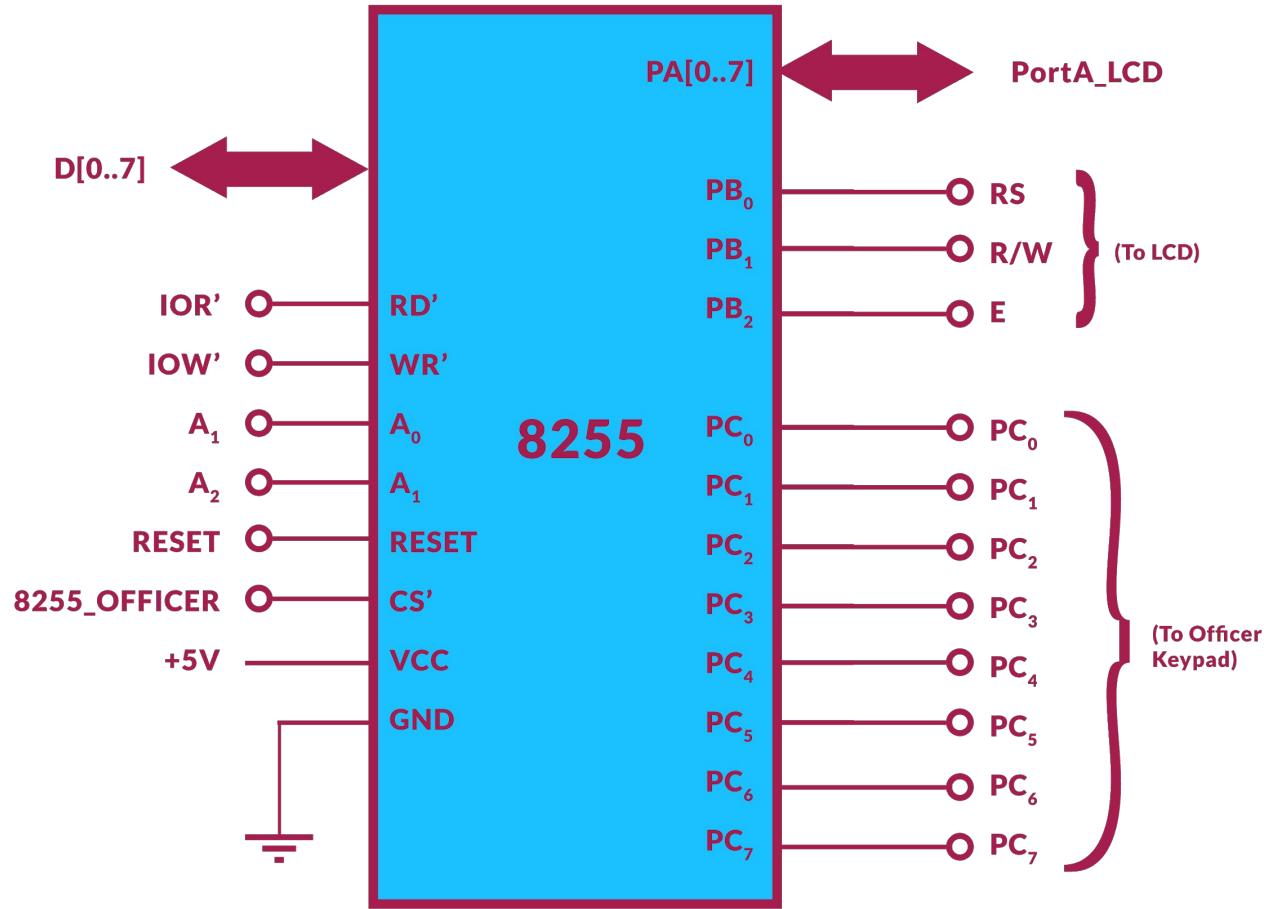

Officer Side 8255

Addresses:

Port A @ 00h

Port B @ 02h

Port C @ 04h


Control Reg @ 06h

I/O Devices:


Port A: LCD Data-lines

Port B: LCD Control-Lines


Port C: Officer's Hex Keypad

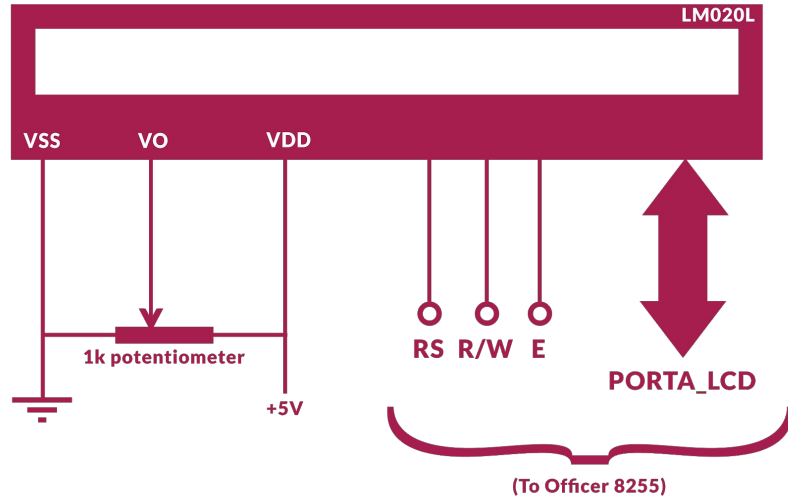

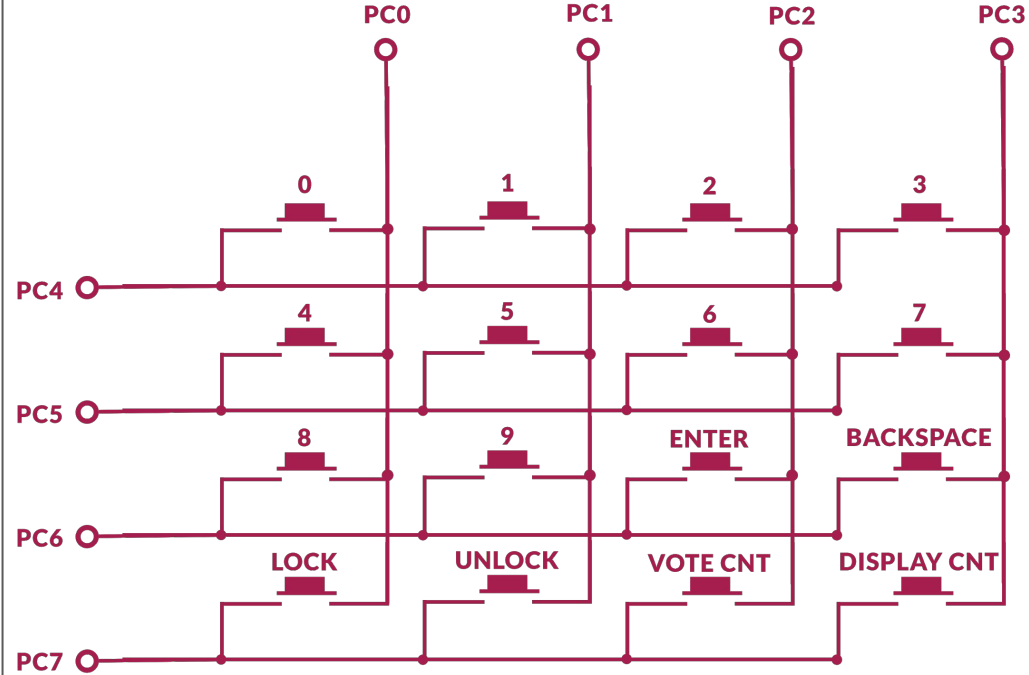16x1 LCD Display (to Port A and B of Officer 8255)
(LM020L)



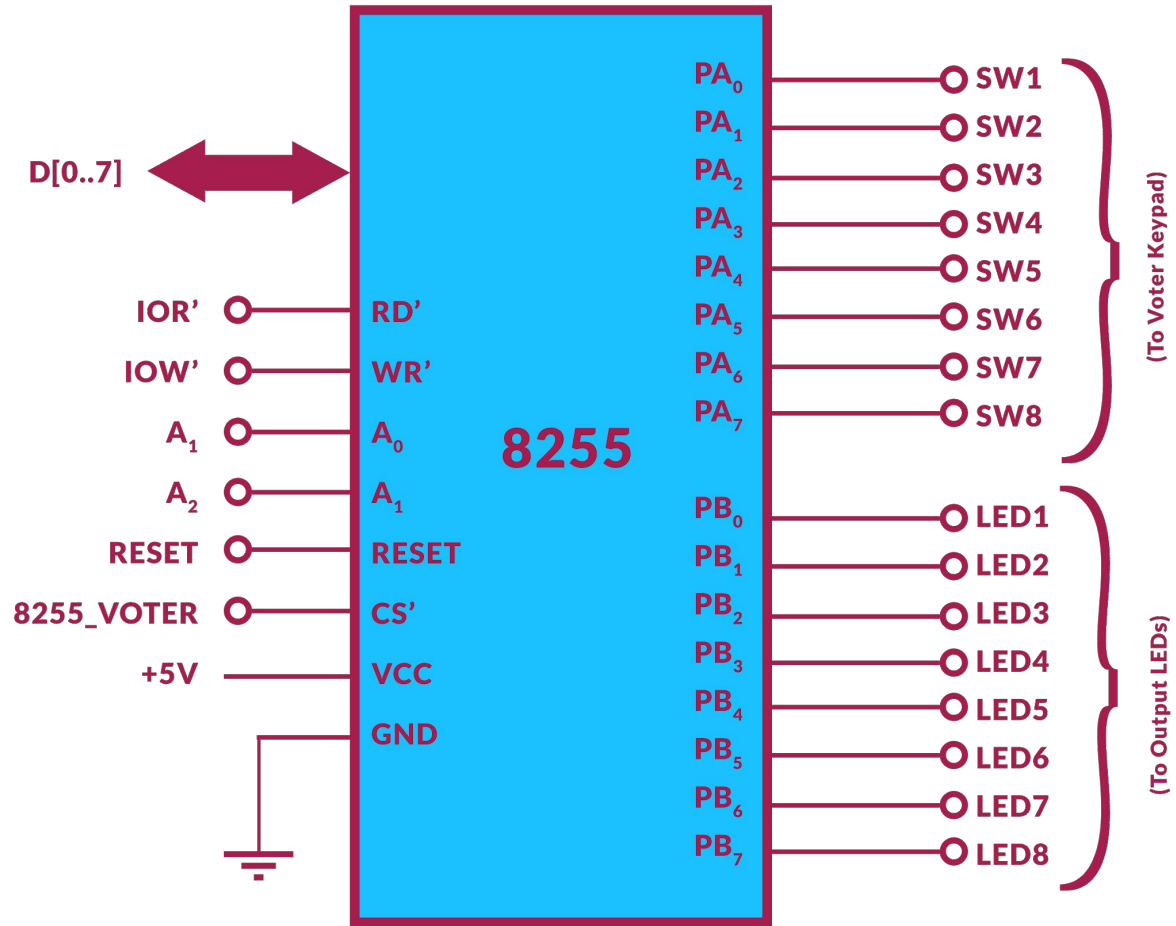Officer's Hex Keypad (to Port C of Officer 8255)



Voters' side 8255

Addresses:

Port A @ 10h

Port B @ 12h

Port C @ 14h


Control Reg @ 16h

I/O Devices:


Port A: One-hot voter buttons

Port B: One-hot Output LEDs

Port C: *unused*

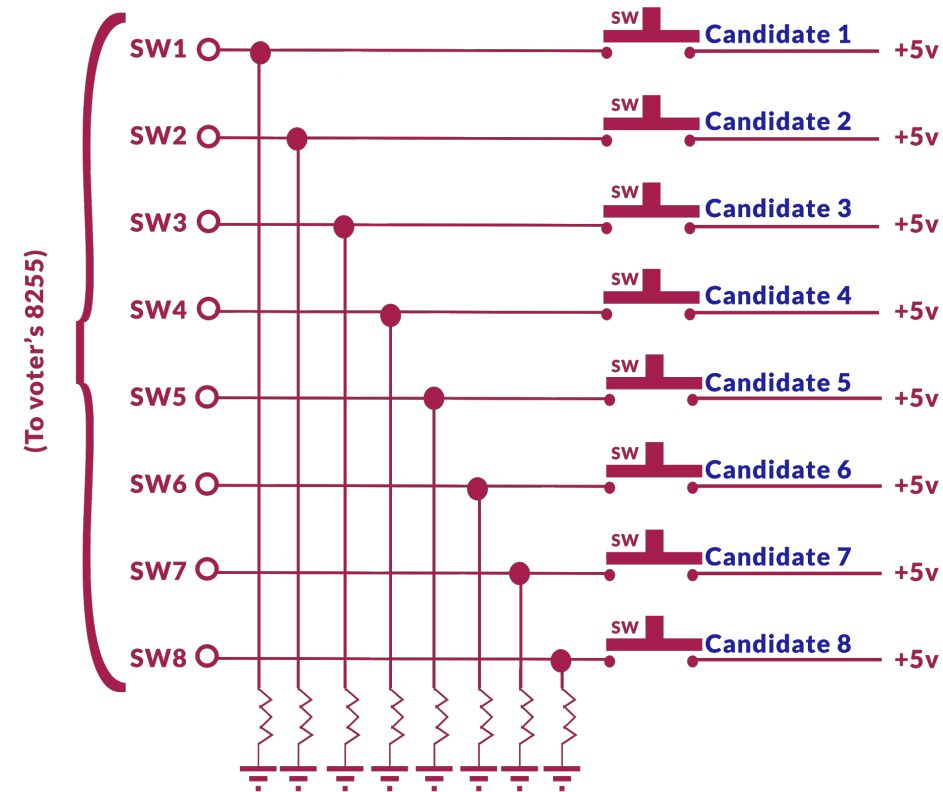

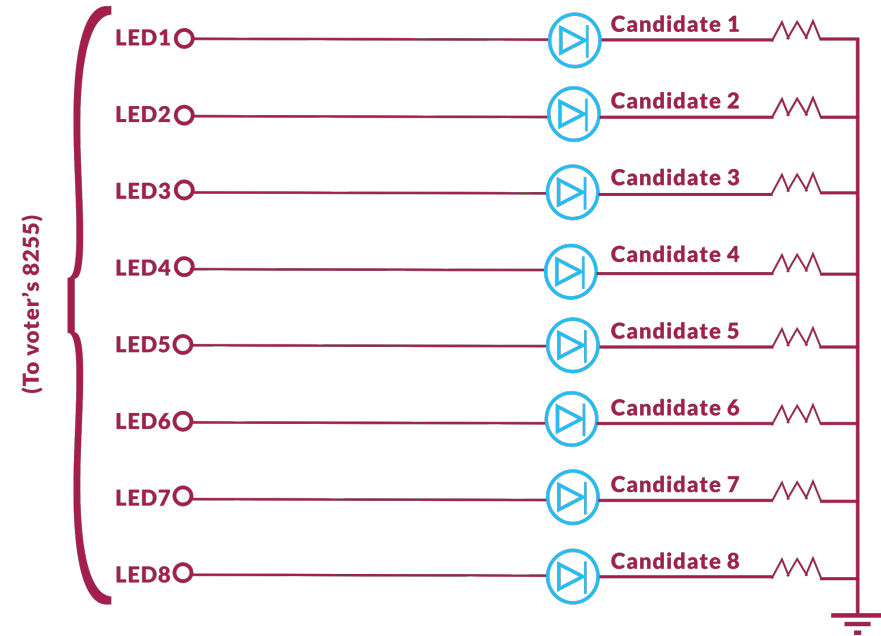Voter's Input buttons (to Port A of Voter's 8255)



Output LEDs (to Port B of Voter's 8255)

Configuration:

Counter 0: Mode 2 (Count=50,000d)

Counter 1: Mode 2 (Count=100d)


Counter 2: Mode 0 (Count=36,000d)

Outputs:

OUT 0 @ 100Hz

OUT 1 @ 1Hz

OUT 2 @ 1/10 Hours

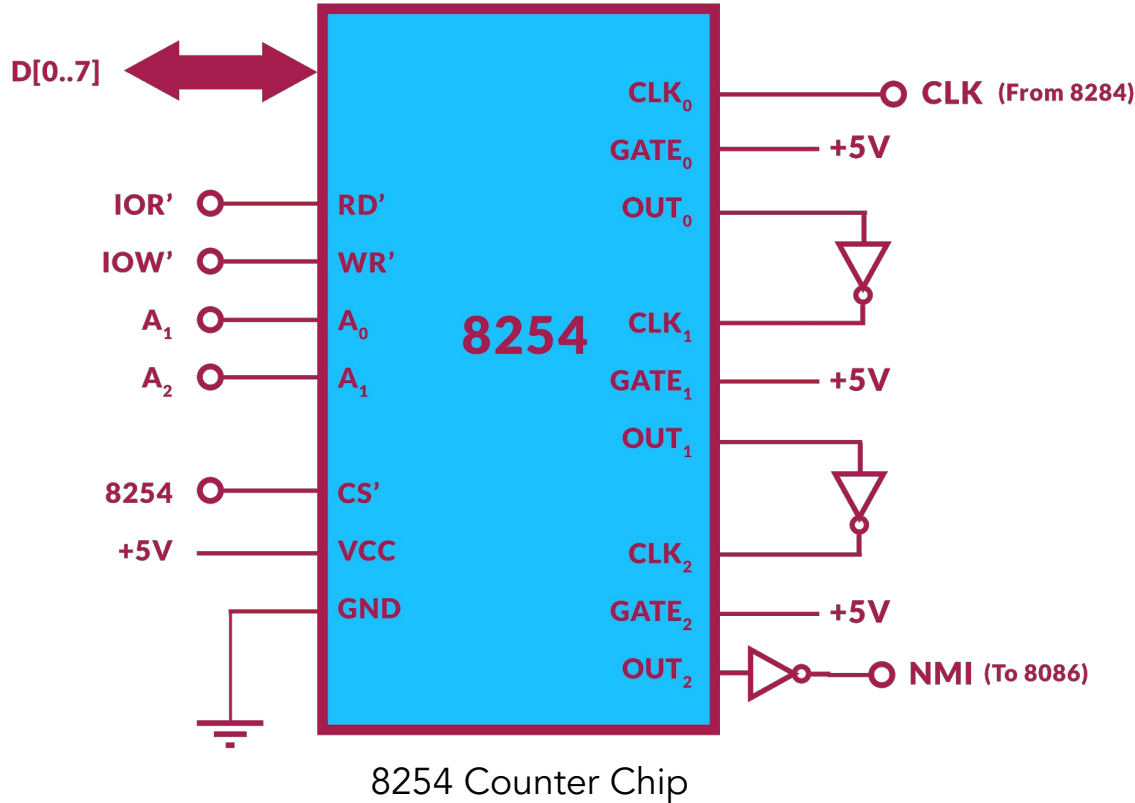

Addresses:

Counter 0 @ 20h

Counter 1 @ 22h

Counter 2 @ 24h

Control Reg @ 26h